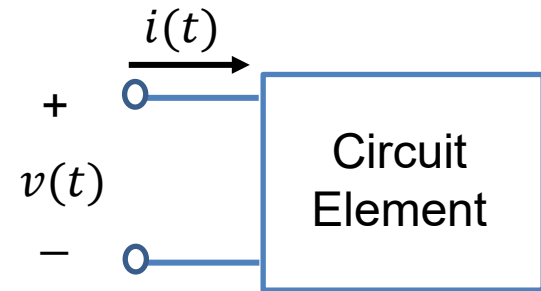


Power in AC Circuits

When voltages and currents are sinusoids, power will be a function of time.

$$p(t) = i(t)v(t)$$


We refer to $p(t)$ as the *instantaneous power*.



Writing $i(t)$ and $v(t)$ explicitly as sinusoids:

$$i(t) = I_m \cos(\omega t + \theta_i),$$
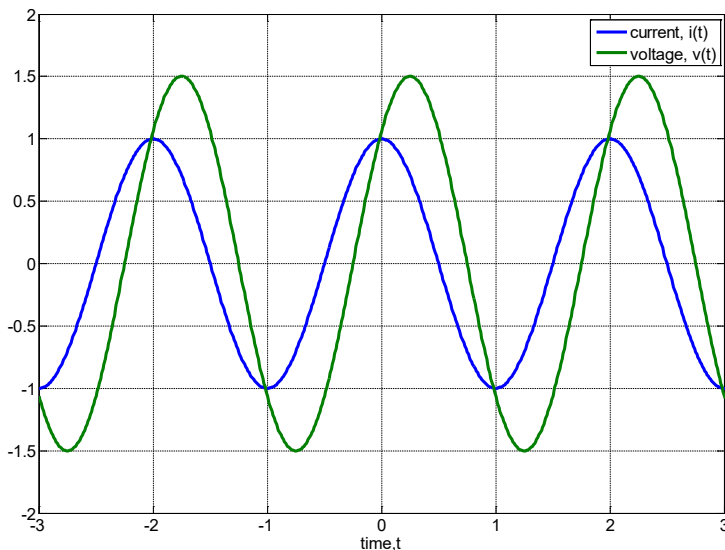
$$v(t) = V_m \cos(\omega t + \theta_v).$$



It is common to define a time reference so that the current has a positive maximum at $t = 0$.

In that case, both $i(t)$ and $v(t)$ must be shifted by θ_i so that:

$$i(t) = I_m \cos(\omega t),$$

$$v(t) = V_m \cos(\omega t + \theta_v - \theta_i).$$

Power in AC Circuits

Using the time reference convention from the previous slide, the instantaneous power becomes:

$$p(t) = i(t)v(t) \\ = I_m V_m \cos(\omega t) \cos(\omega t + \theta_v - \theta_i)$$

$$= \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \\ + \frac{I_m V_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

$$= \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \\ + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) \\ - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$

Use the trig identity:


$$\cos(x) \cos(y) \\ = \frac{1}{2} \cos(x + y) + \frac{1}{2} \cos(x - y)$$

Use the trig identity:

$$\cos(x + y) \\ = \cos(x) \cos(y) - \sin(x) \sin(y)$$

Power in AC Circuits
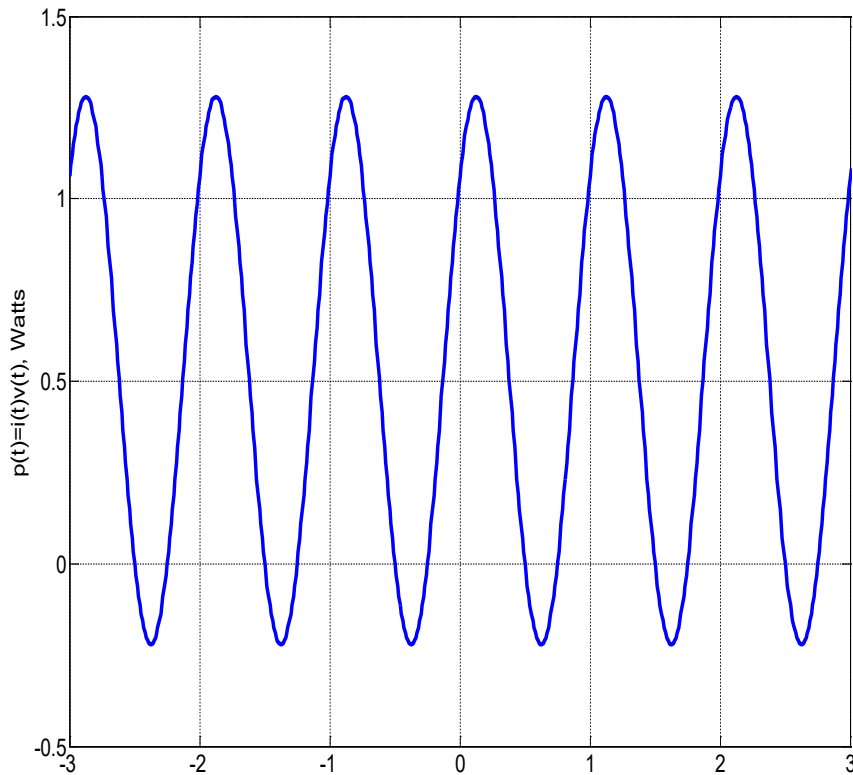
$$p(t) = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$



Some observations:

- Instantaneous power oscillates at twice the frequency of current/voltage.
- Instantaneous power can be negative, even though we are using passive elements.

- The average value of the instantaneous power is

$$P = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i)$$

- Average power will be positive and depends not only on the peak current and voltage but also on the phase relationship between them.

Average and Reactive Power

$$p(t) = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$

Some Definitions:

- *Average Power* or *Real Power*, measured in Watts

$$P = \langle p(t) \rangle = \frac{1}{T} \int_{t_o}^{t_o+T} p(t) dt = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i).$$

- *Reactive Power*, measured in VARs (volt-amp-reactive)

$$Q = \frac{I_m V_m}{2} \sin(\theta_v - \theta_i).$$

With these definitions, instantaneous power is written as:

$$p(t) = P + P \cos(2\omega t) - Q \sin(2\omega t).$$

Average and Reactive Power


Resistors

$$\theta_v = \theta_i,$$

$$\cos(\theta_v - \theta_i) = 1, \sin(\theta_v - \theta_i) = 0.$$

$$P = \frac{I_m V_m}{2}, Q = 0.$$

$$p(t) = P + P \cos(2\omega t).$$

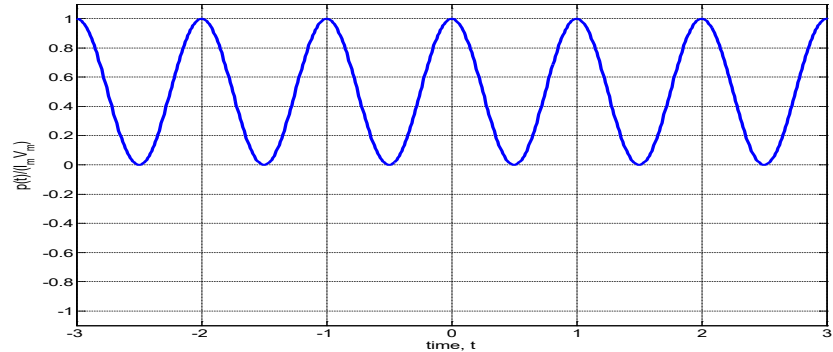


Inductors

$$\theta_v = \theta_i + 90^\circ,$$

$$\cos(\theta_v - \theta_i) = 0, \sin(\theta_v - \theta_i) = 1.$$

$$P = 0, Q = \frac{I_m V_m}{2}.$$
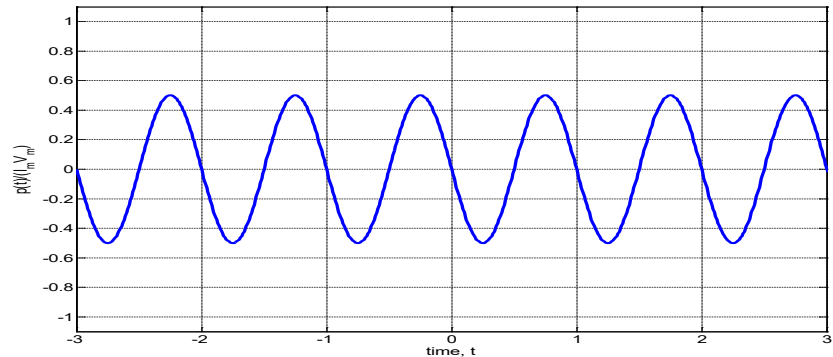
$$p(t) = -\frac{I_m V_m}{2} \sin(2\omega t).$$




Capacitors

$$\theta_v = \theta_i - 90^\circ,$$

$$\cos(\theta_v - \theta_i) = 0, \sin(\theta_v - \theta_i) = -1.$$

$$P = 0, Q = -\frac{I_m V_m}{2}.$$

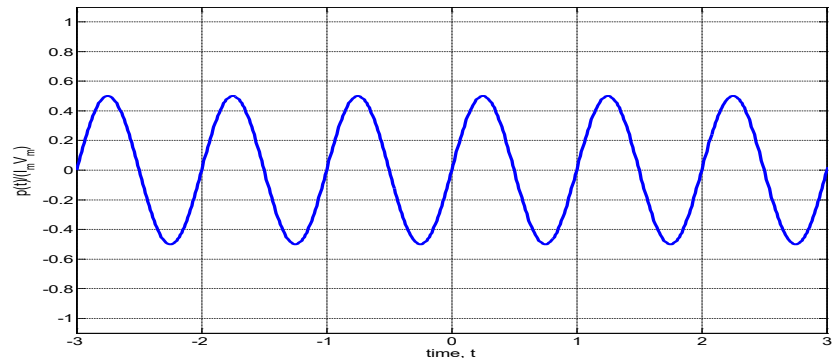
$$p(t) = +\frac{I_m V_m}{2} \sin(2\omega t).$$



Power Factors and Reactive Factors

More Definitions:

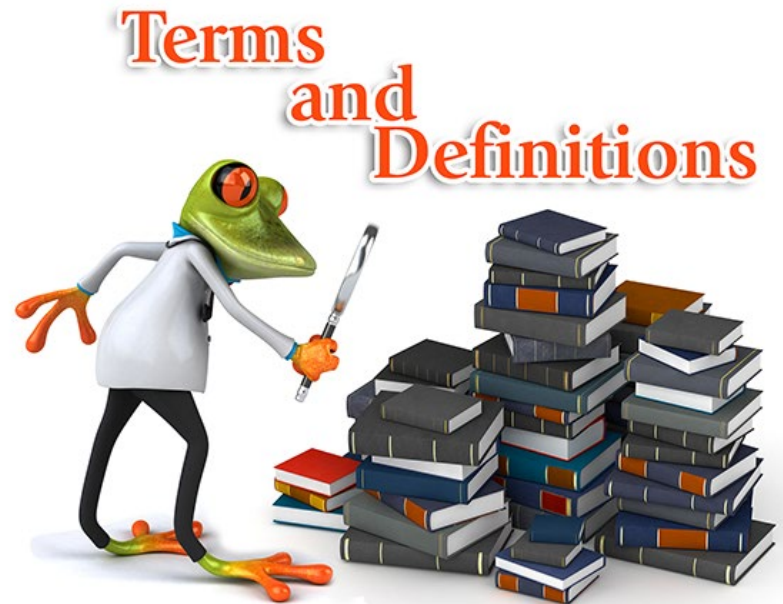
- $\theta_v - \theta_i =$ power factor angle
- $\cos(\theta_v - \theta_i) =$ power factor (pf)
- $\sin(\theta_v - \theta_i) =$ reactive factor (rf)
- $\theta_v > \theta_i \rightarrow$ lagging power factor
current lags voltage
 $rf > 0$
inductive element
- $\theta_v < \theta_i \rightarrow$ leading power factor
current leads voltage
 $rf < 0$
capacitive element



Example

Find:

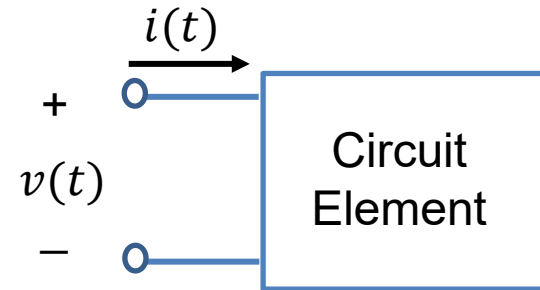- (a) Average power, P .
- (b) Reactive power, Q .
- (c) Power factor, pf .
- (d) Reactive factor, rf .



$$v(t) = 100\cos(\omega t + 15^\circ) \text{ V}$$
$$i(t) = 4\sin(\omega t - 15^\circ) \text{ A}$$

RMS Power

It is common to express power calculations in terms of RMS values. For example, when we say that a wall outlet produces 120V AC, this is actually an RMS value.

Recall that for sinusoidal voltages and currents $V_{rms} = V_m/\sqrt{2}$ and $I_{rms} = I_m/\sqrt{2}$. Then:

$$\begin{aligned}P &= I_{rms} V_{rms} \cos(\theta_v - \theta_i), \\Q &= I_{rms} V_{rms} \sin(\theta_v - \theta_i).\end{aligned}$$

In a resistor,

$$\begin{aligned}P &= I_{rms} V_{rms}, \\V_{rms} &= I_{rms} R,\end{aligned}$$

so that formulas for average power correspond to what we are used to for DC circuits:

$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R}.$$

Power in AC Circuits Using Phasors


It is sometimes convenient to use phasors to compute various power quantities. To aid in this, define a “complex power” which is a complex number formed from average and reactive power.

Complex Power, measured in VAs (volt-amps)

$$S = P + jQ$$

Apparent Power, measured in VAs (volt-amps)

$$|S| = \sqrt{P^2 + Q^2}.$$

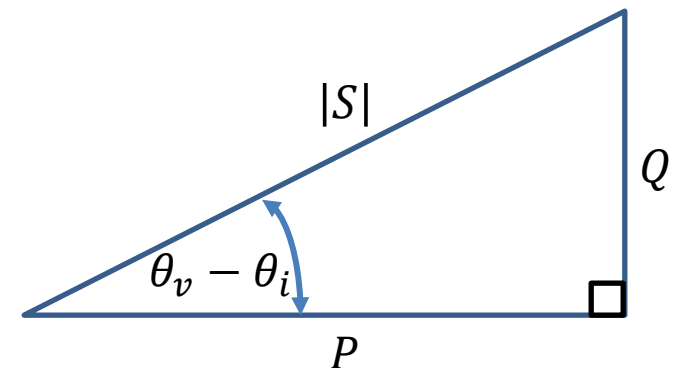

You can visualize all of these quantities with a right triangle as shown.

Note: If any two of the quantities in the figure above are known, the others can be found using the appropriate trig/geometry.

Power in AC Circuits Using Phasors

Recalling the definitions of P , Q , S , complex power can be written as


$$\begin{aligned} S &= P + jQ \\ &= \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + j \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \end{aligned}$$

$$= \frac{I_m V_m}{2} \exp(j(\theta_v - \theta_i))$$

$$= \frac{1}{2} (V_m e^{j\theta_v}) (I_m e^{-j\theta_i})$$

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^*$$

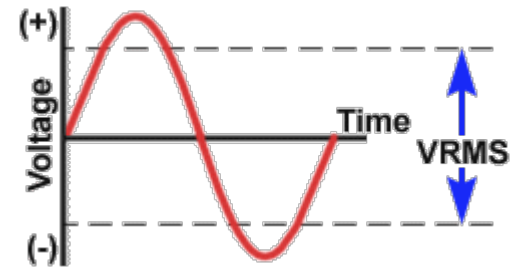We can compute S directly from the voltage and current phasors and the P and Q can be extracted from $\text{Re}[S]$ and $\text{Im}[S]$.



Alternatively, we can use RMS voltages and currents (and phasors):

$$\mathbf{V}_{rms} = V_{rms} e^{j\theta_v} = \frac{V_m}{\sqrt{2}} e^{j\theta_v}$$

$$\mathbf{I}_{rms} = I_{rms} e^{j\theta_i} = \frac{I_m}{\sqrt{2}} e^{j\theta_i}$$

$$S = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$$

Power in AC Circuits Using Phasors

For an element with impedance Z , the voltage and current phasors are related by

$$\mathbf{V}_{rms} = \mathbf{I}_{rms}Z,$$

so that various forms of the power expressions can be developed.

$$\begin{aligned} S &= \mathbf{V}_{rms} \mathbf{I}_{rms}^* \\ &= (\mathbf{I}_{rms}Z) \mathbf{I}_{rms}^* \\ &= |\mathbf{I}_{rms}|^2 Z \\ &= |\mathbf{I}_{rms}|^2 (X + jY) \end{aligned}$$

Therefore,

$$\begin{aligned} P &= |\mathbf{I}_{rms}|^2 X, \\ Q &= |\mathbf{I}_{rms}|^2 Y. \end{aligned}$$

$$\begin{aligned} S &= \mathbf{V}_{rms} \mathbf{I}_{rms}^* \\ &= \mathbf{V}_{rms} \left(\frac{\mathbf{V}_{rms}}{Z} \right)^* = \frac{|\mathbf{V}_{rms}|^2}{Z^*} \\ &= \frac{|\mathbf{V}_{rms}|^2}{X - jY} = \frac{|\mathbf{V}_{rms}|^2 (X + jY)}{X^2 + Y^2} \end{aligned}$$


Therefore,

$$\begin{aligned} P &= \frac{|\mathbf{V}_{rms}|^2 X}{|Z|^2}, \\ Q &= \frac{|\mathbf{V}_{rms}|^2 Y}{|Z|^2}. \end{aligned}$$

Example

Find:

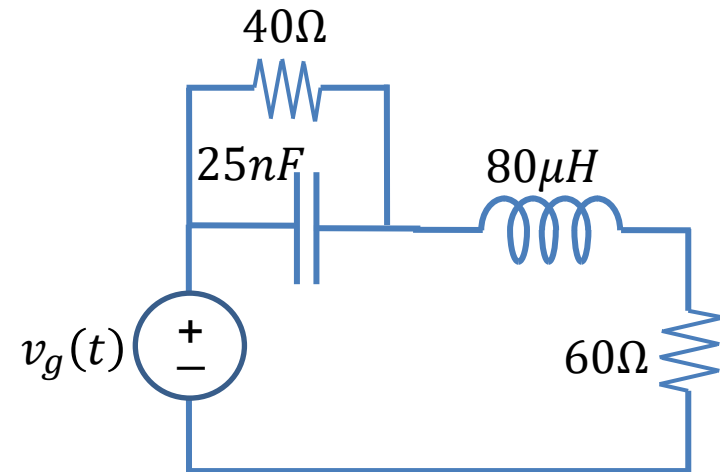- (a) Average power,
 - (b) Reactive power,
 - (c) Apparent power,
- Supplied by the voltage source.



$$v_g(t) = 40\cos(10^6 t) \text{ V}$$