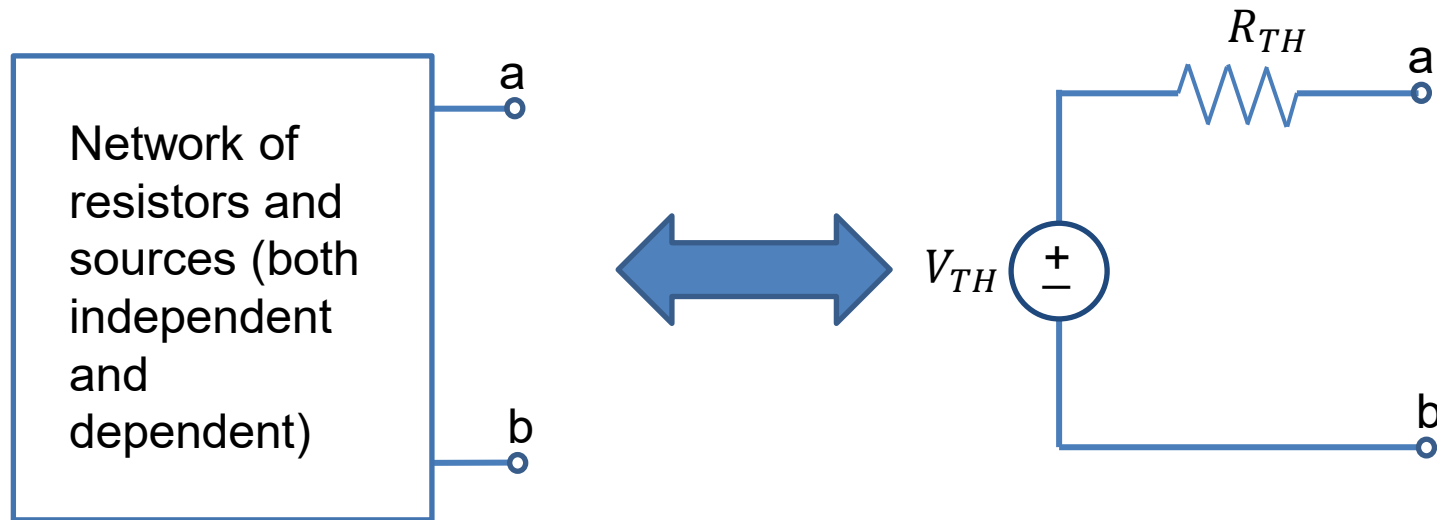


# Thevenin Equivalent Circuits

A complicated circuit of sources and resistive elements can be reduced to a single voltage source in series with a resistor to study how the circuit will behave with respect to a load. This is known as a **Thevenin equivalent circuit**.





**Q:** How do we find the values of  $V_{TH}$  and  $R_{TH}$  so the equivalence holds?

**A:** Since there are only two unknowns, any two measurements that we can make on our circuit, should provide enough information to infer the Thevenin Equivalent circuit.
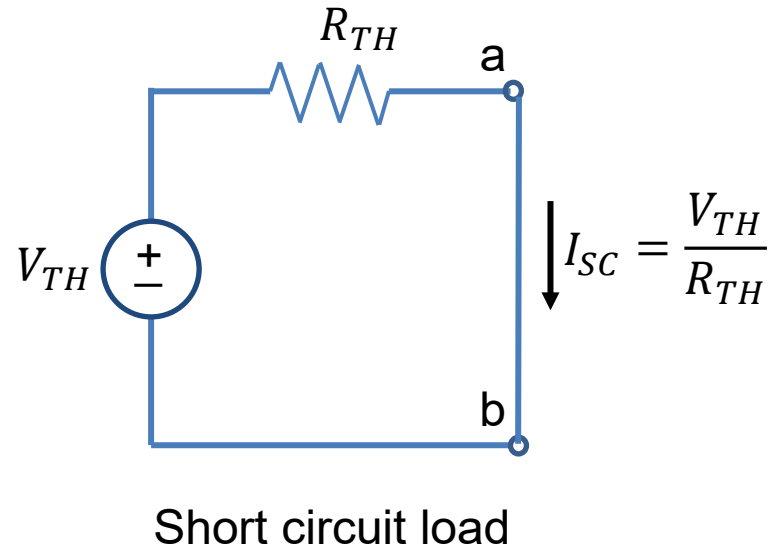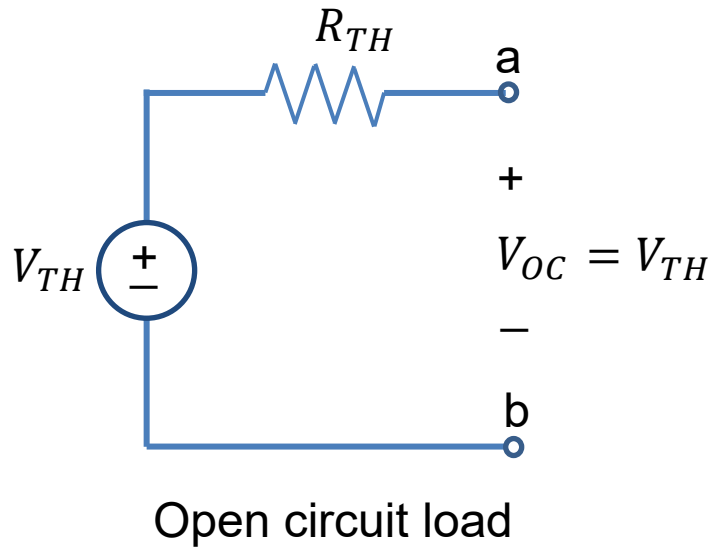
# Thevenin Equivalent Circuits

In order to find the appropriate values of  $V_{TH}$  and  $R_{TH}$ , consider loading the circuit with either an open circuit or a short circuit.




From the two relationships above, the Thevenin equivalent circuit can be found from the open circuit voltage,  $V_{OC}$ , and the short circuit current,  $I_{SC}$ .

$$V_{TH} = V_{OC} \text{ and } R_{TH} = \frac{V_{OC}}{I_{SC}}$$

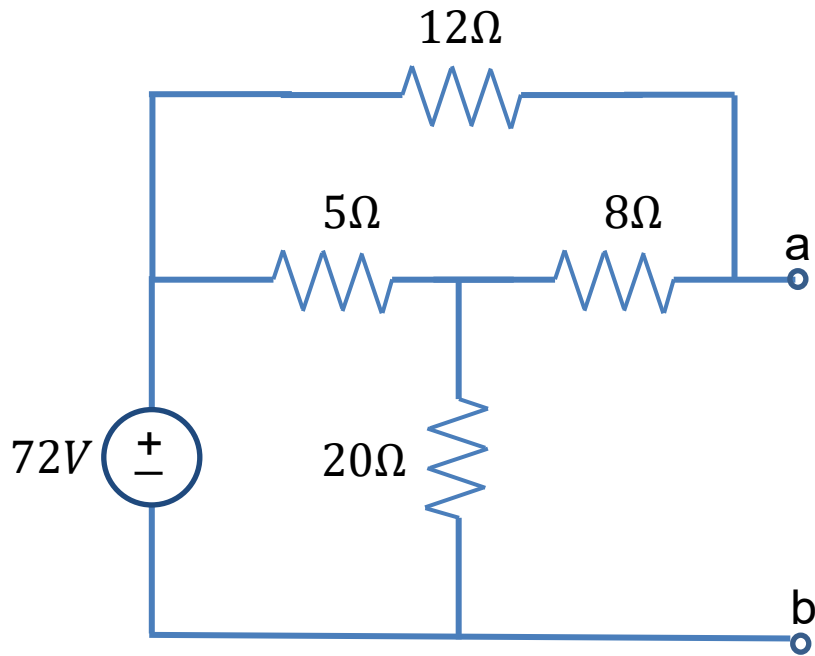
# Example

Find the Thevenin equivalent with respect to the terminals a-b.



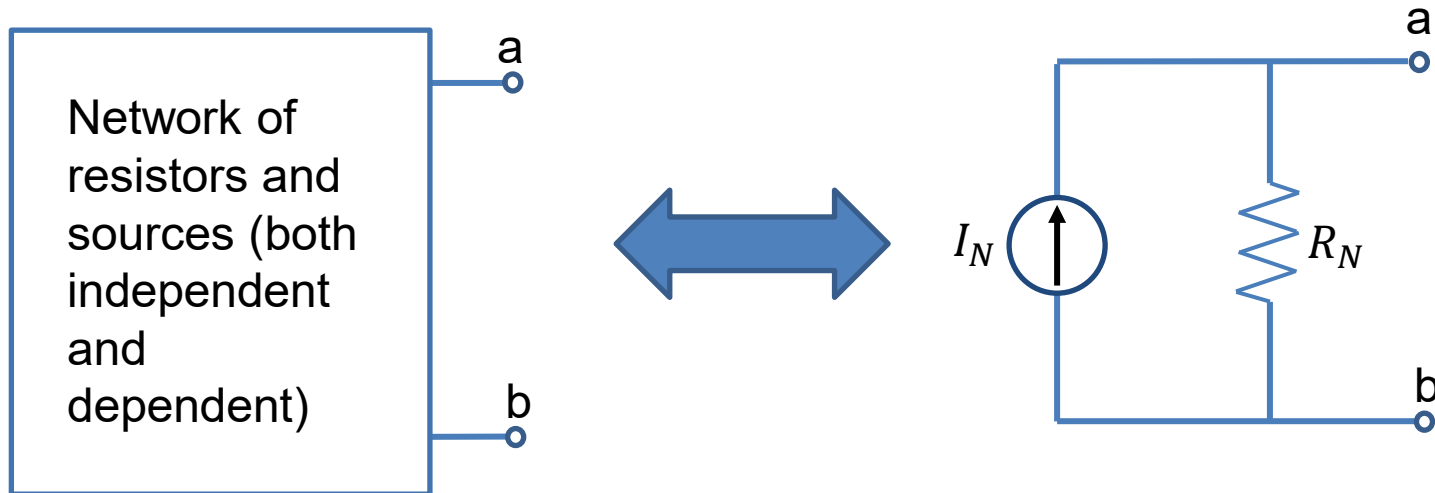
# Norton Equivalent Circuits

Similar to a Thevenin equivalent circuit, we can also construct a **Norton equivalent circuit** which consists of a current source in parallel with a resistor.



$$V_{OC} = I_N R_N$$

$$I_{SC} = I_N$$

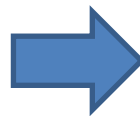

$$I_N = I_{SC}$$

$$R_N = \frac{V_{OC}}{I_{SC}}$$



same as  $R_{TH}$

# Thevenin/Norton Equivalent Circuits

There are a number of techniques we can use to find a Thevenin/Norton equivalent circuit.

**Method 1:** Use source transformations and serial/parallel combinations to reduce the circuit to its Thevenin or Norton equivalent.

**Method 2:** Find the open circuit voltage and the short circuit current. Then use:


$$V_{TH} = V_{OC}, I_N = I_{SC}, R_{TH} = R_N = \frac{V_{OC}}{I_{SC}}$$

**Method 3:** For circuits with no dependent sources,  $R_{TH}$  can be found by disabling all independent sources ( $V = 0 \rightarrow$  short,  $I = 0 \rightarrow$  open) and computing the equivalent resistance as seen across the load terminals.

**Note:** Method 3 does not actually find the entire equivalent circuit. It only provides a shortcut for finding  $R_{TH}$  so that you only need to find  $V_{OC}$  **or**  $I_{SC}$  (not both) when using Method 2.
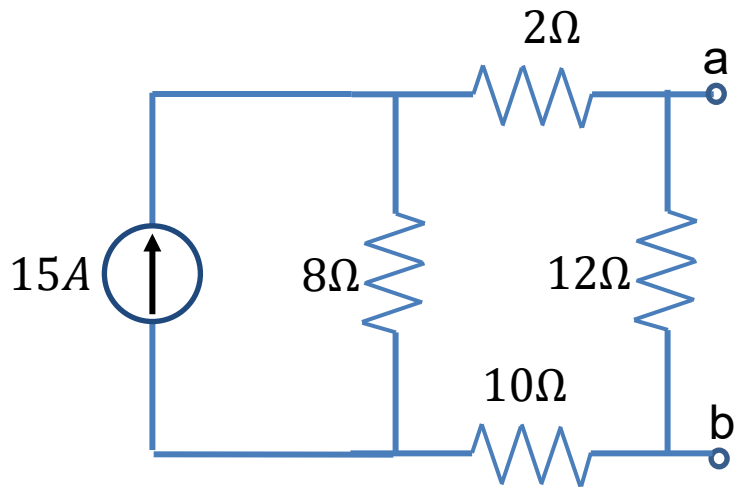
## Example


Find the Thevenin and Norton equivalent circuits with respect to the terminals a-b.


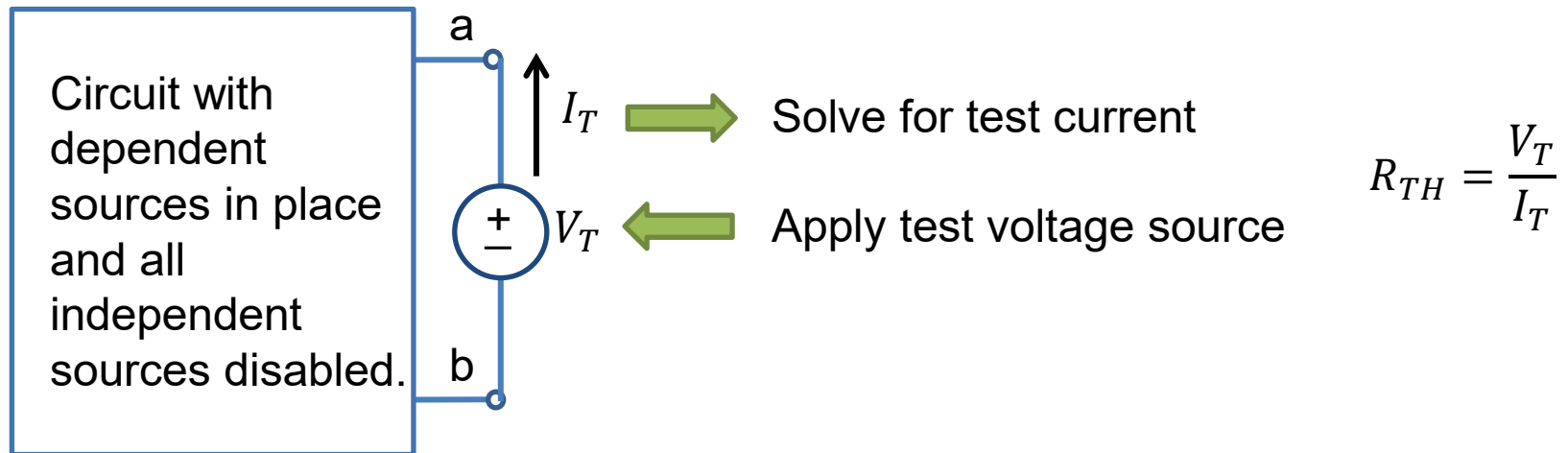
# Thevenin/Norton Equivalent Circuits

For circuits with dependent sources, a modified version of Method 3 can be used.

**Method 3 (modified):** Disable all independent sources. Apply a test source to the load (either  $V_T$  or  $I_T$ ) and then find  $I_T$  or  $V_T$  so that  $R_{TH} = \frac{V_T}{I_T}$ .



# Example

Find the Thevenin equivalent with respect to the terminals a-b.

