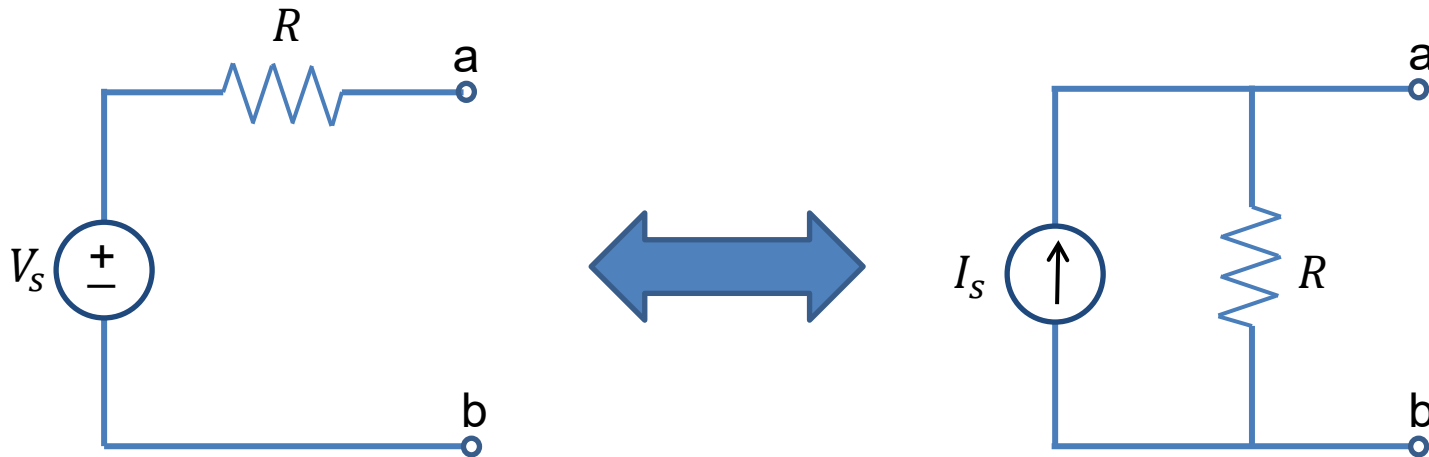


# Source Transformations


Often it is useful to transform a series combination of a voltage source and a resistor to an equivalent current source and a resistor (or vice versa) as shown below.




The equivalency is with respect to the behavior of any load we place across the terminals a-b.

In the next slide we examine the relationship that  $V_s$  and  $I_s$  must have in order for this equivalency to be valid.

# Source Transformations

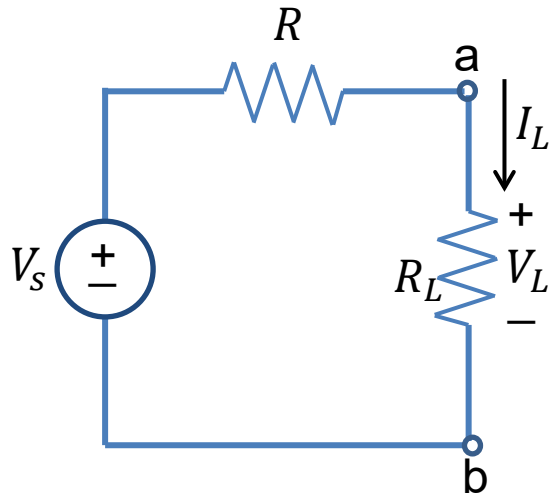
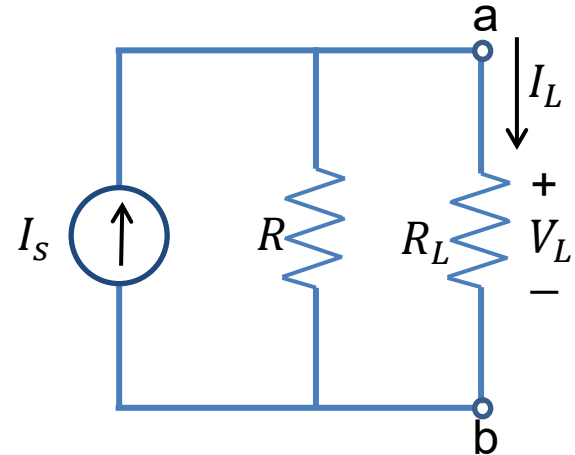
$$I_L = \frac{V_s}{R + R_L}, \quad V_L = V_s \frac{R_L}{R + R_L}$$



$$I_L = I_s \frac{R}{R + R_L}, \quad V_L = I_s \frac{R \cdot R_L}{R + R_L}$$


These equations (and hence the circuits) are equivalent if:

$$V_s = I_s \cdot R$$


We can use this equivalency to simplify the analysis of many circuits.

# Source Transformations

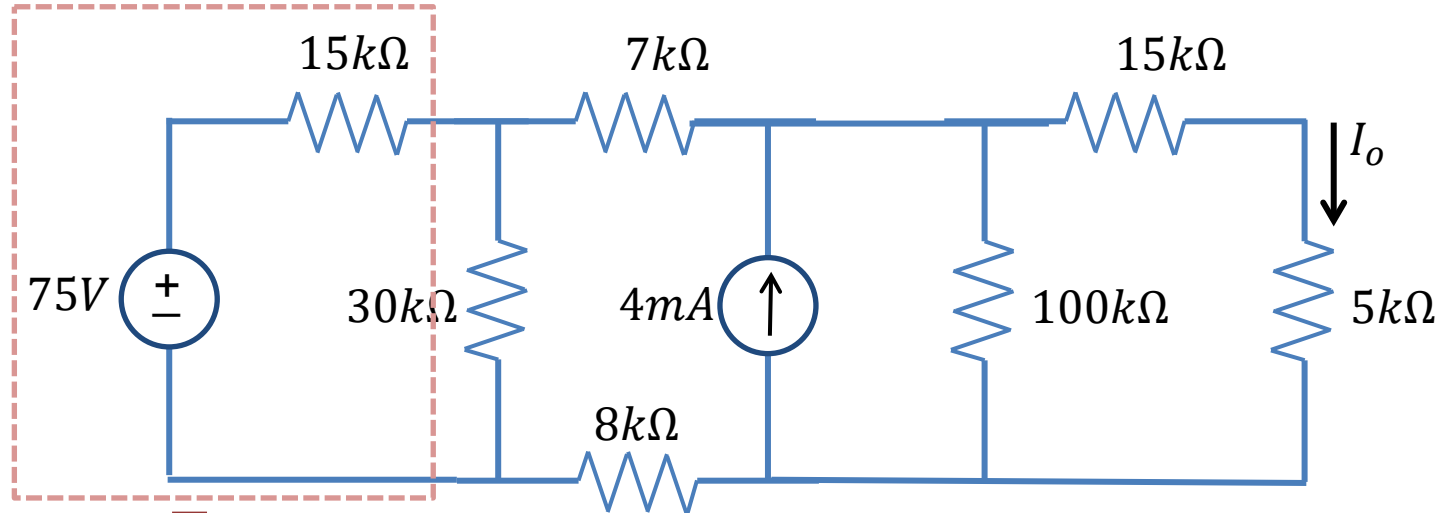
**Example:** Find the current,  $I_o$ , in the  $5k\Omega$  resistor.




First, transform  
voltage source

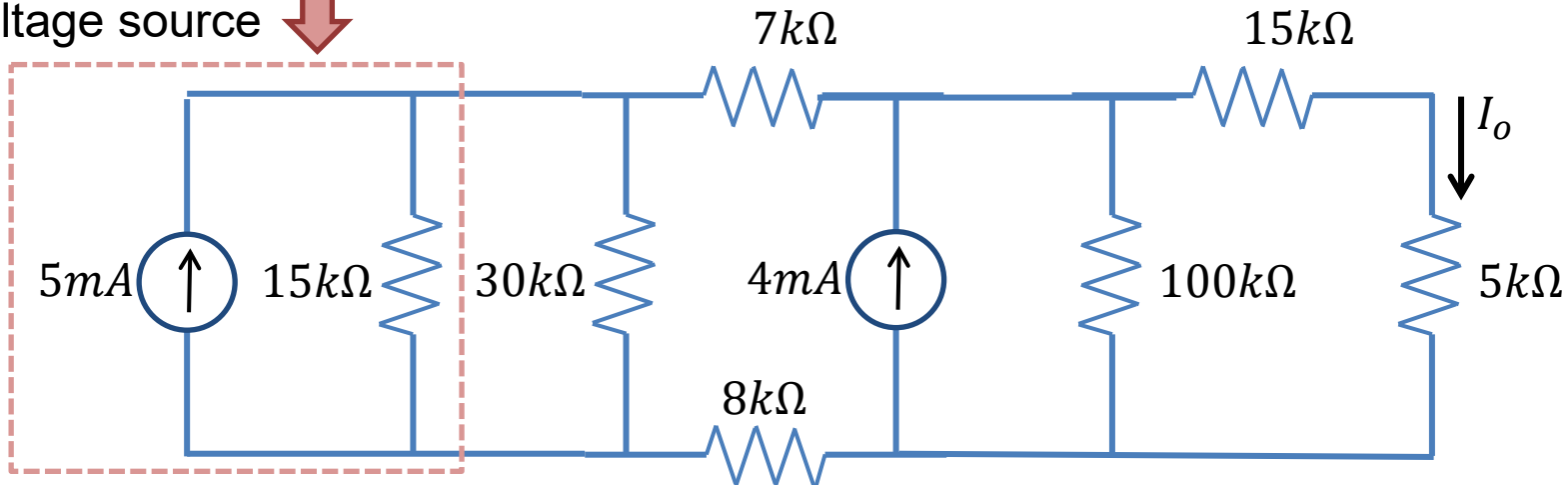


# Source Transformations

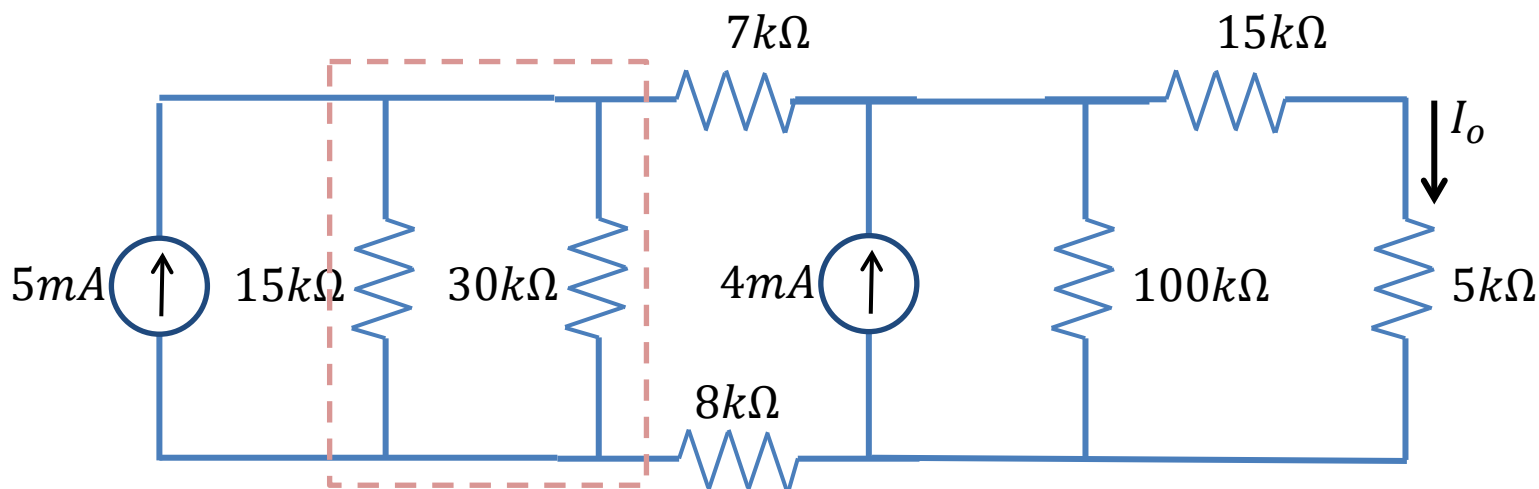


Combine parallel resistors

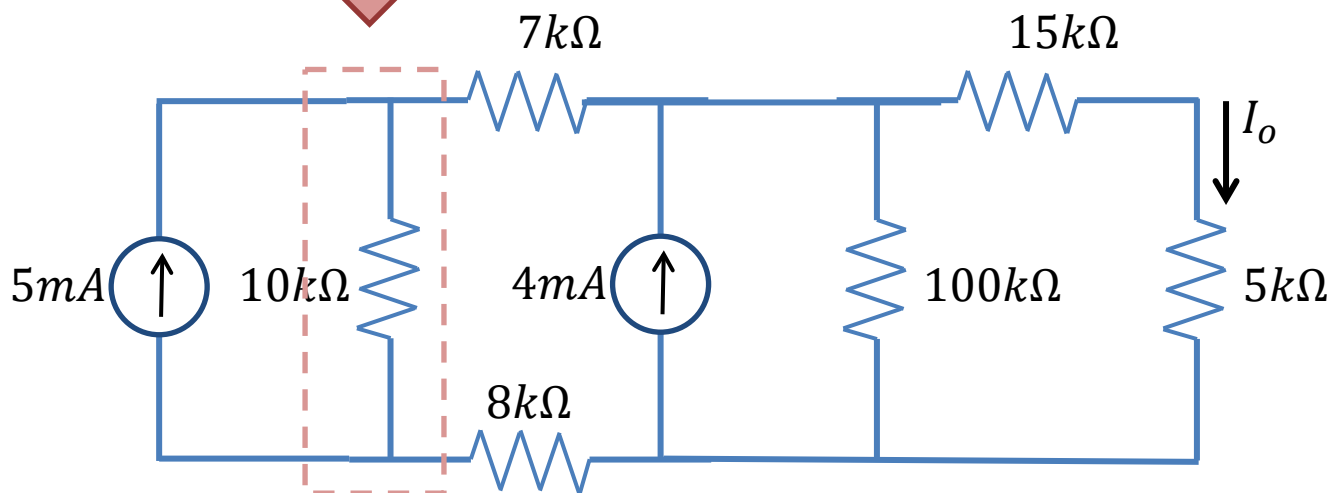


# Source Transformations

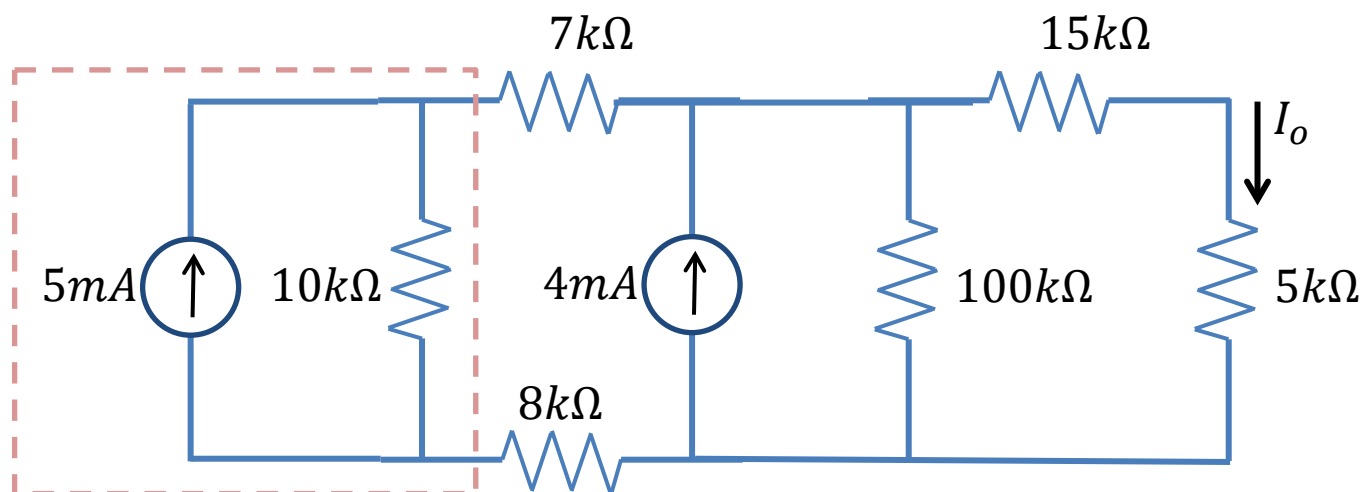


Transform current source

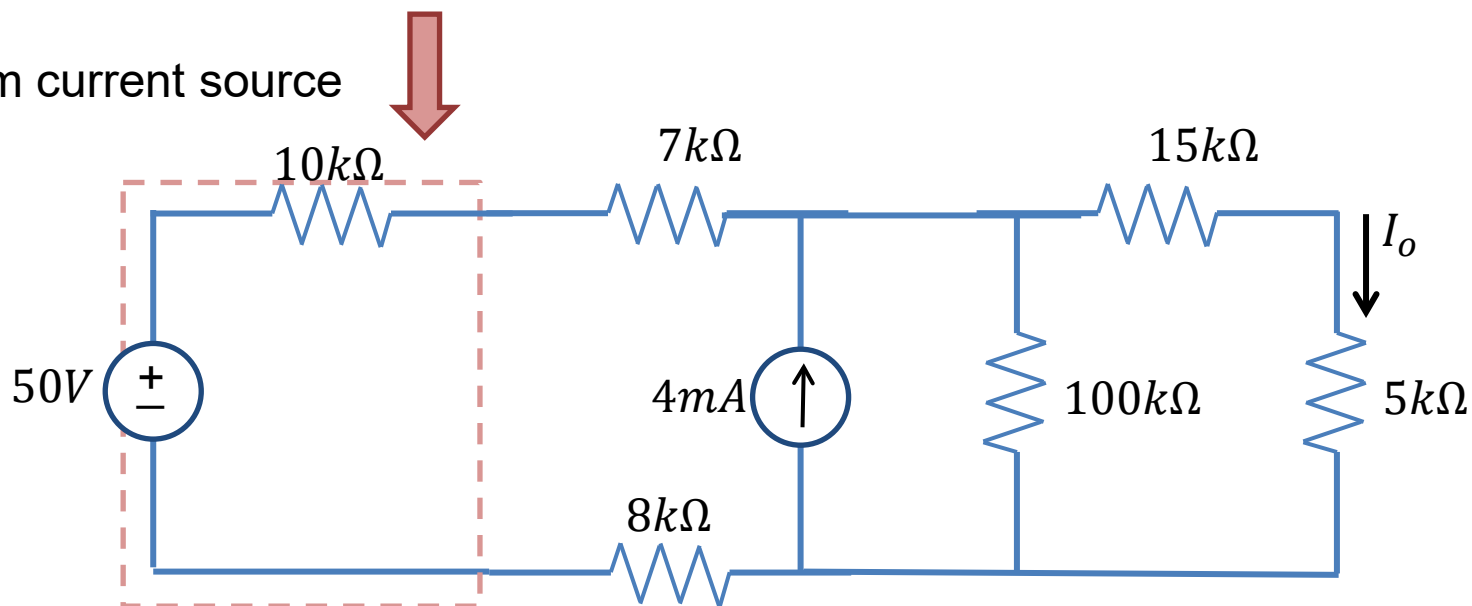


# Source Transformations

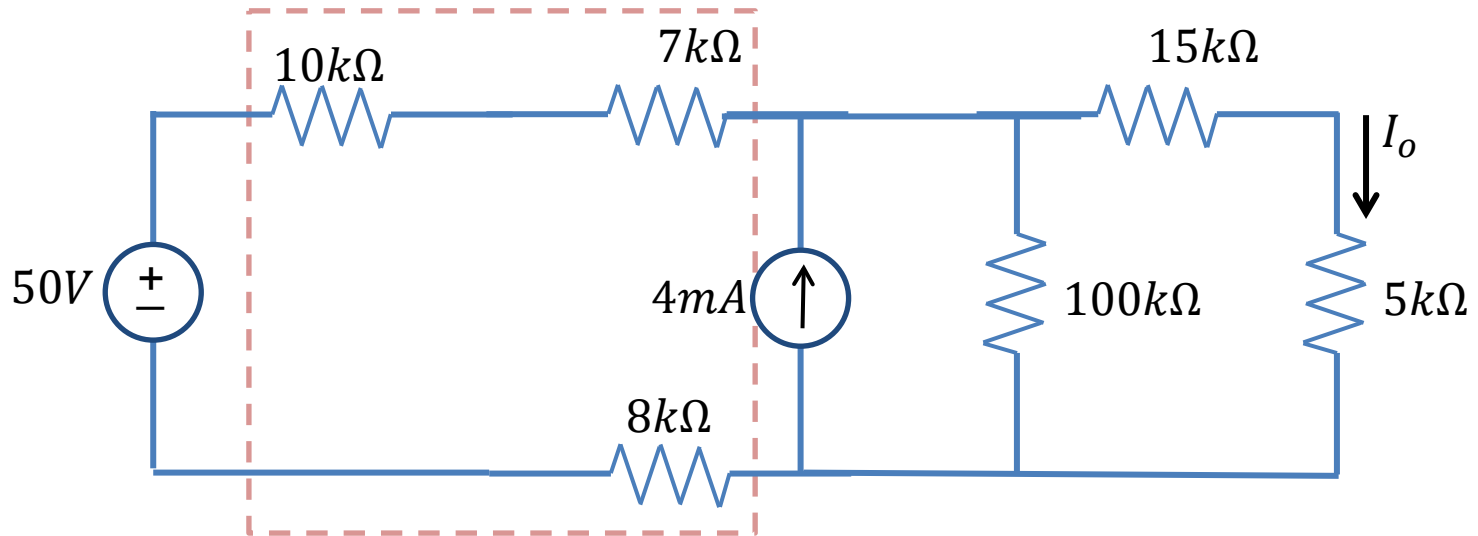


Combine series resistors

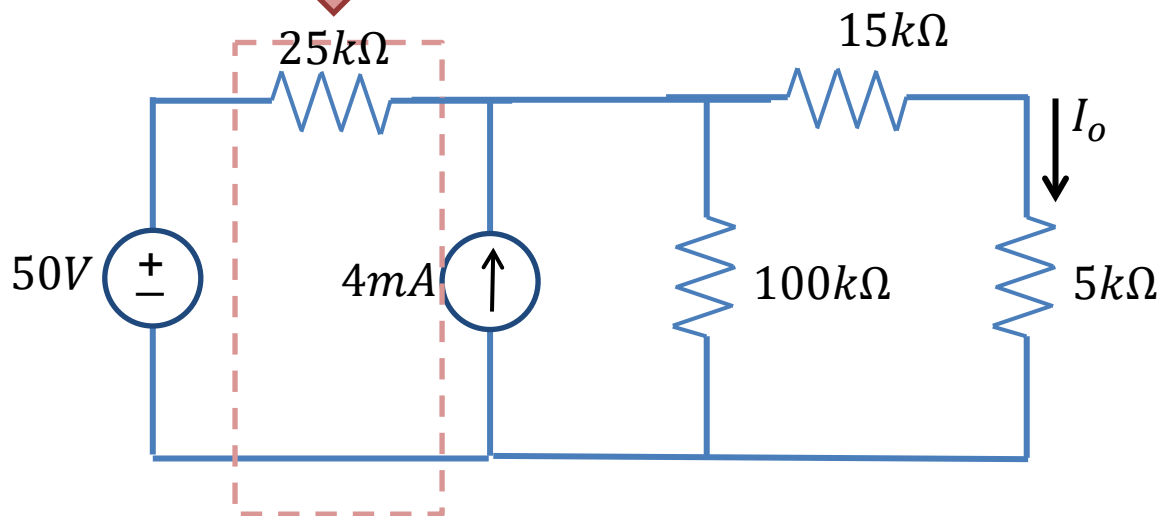


# Source Transformations

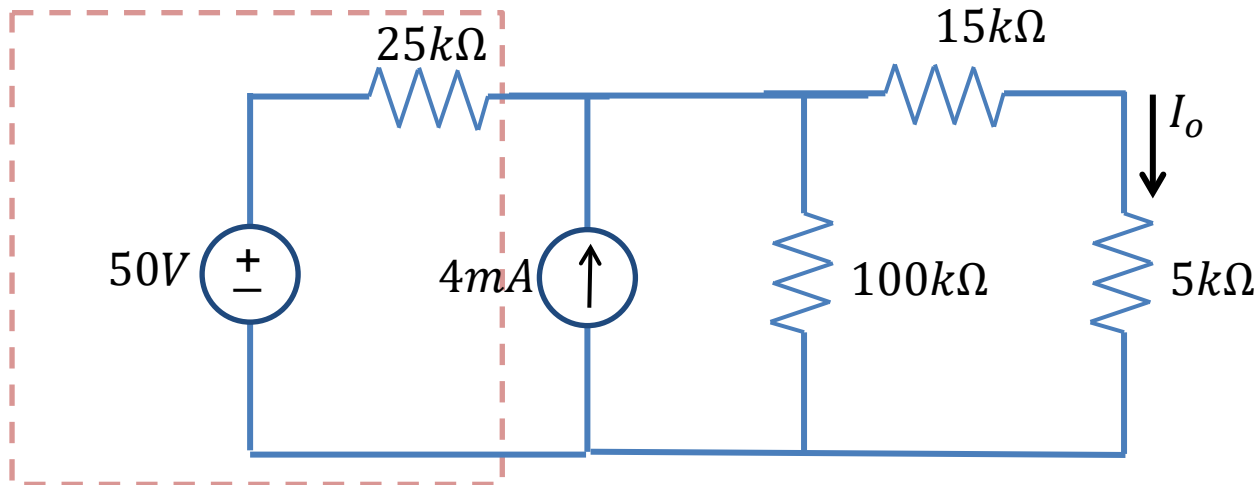


Transform voltage  
source

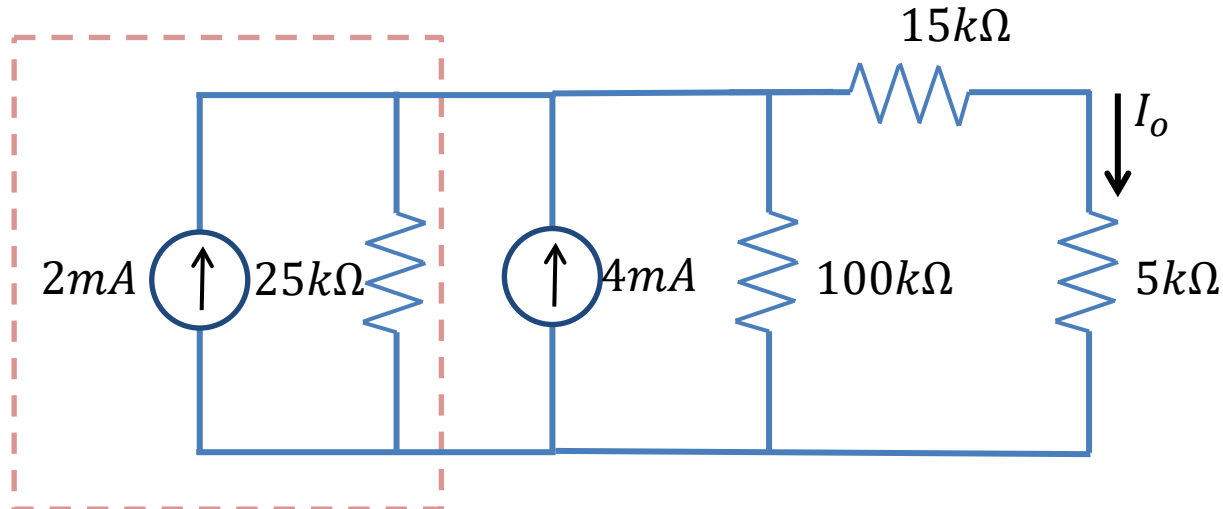

# Source Transformations

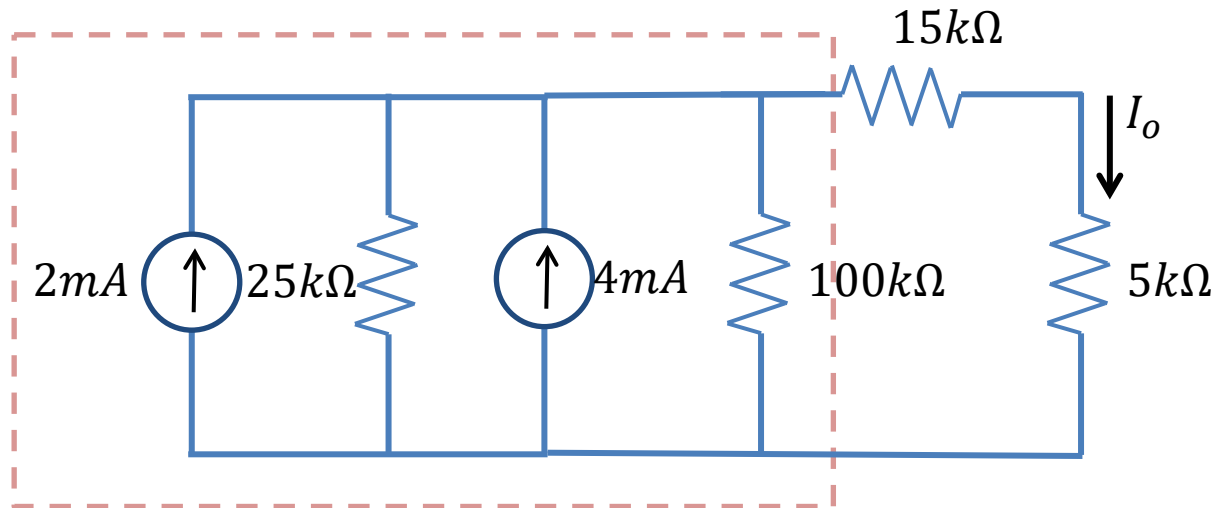


Rearrange  
parallel elements

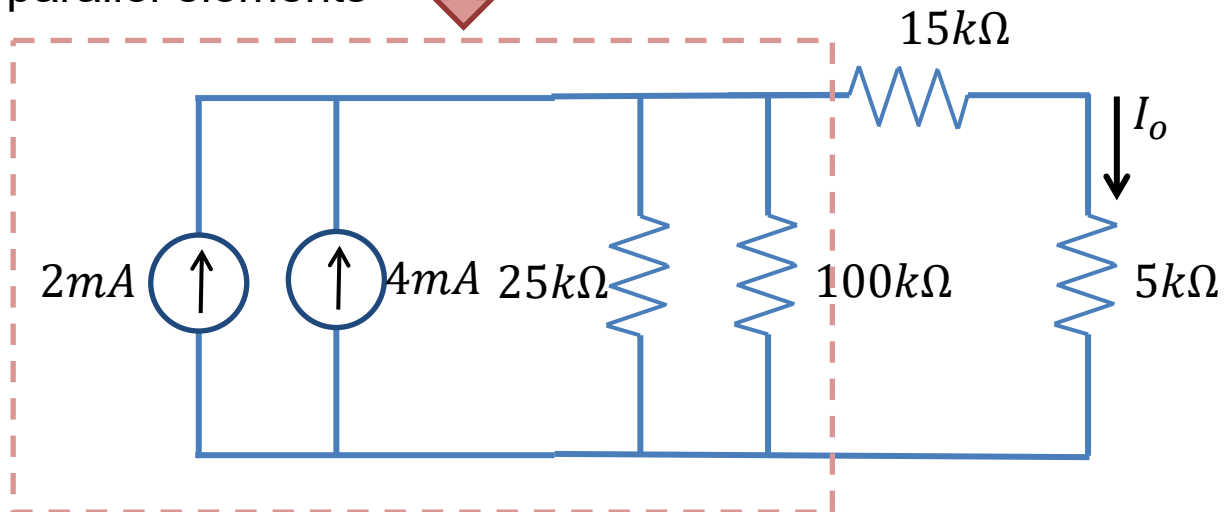




# Source Transformations

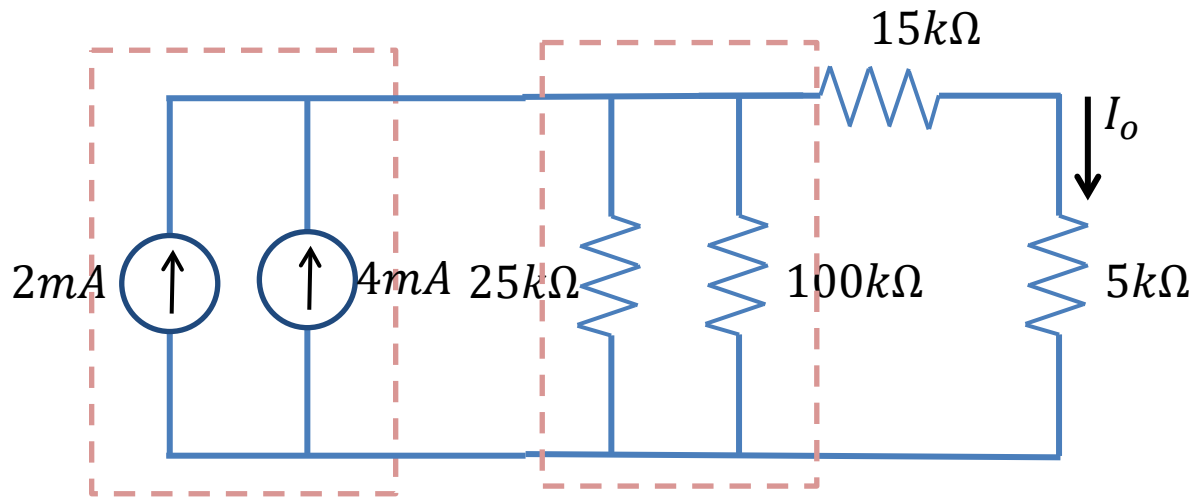


Combine parallel  
current sources




Combine parallel resistors

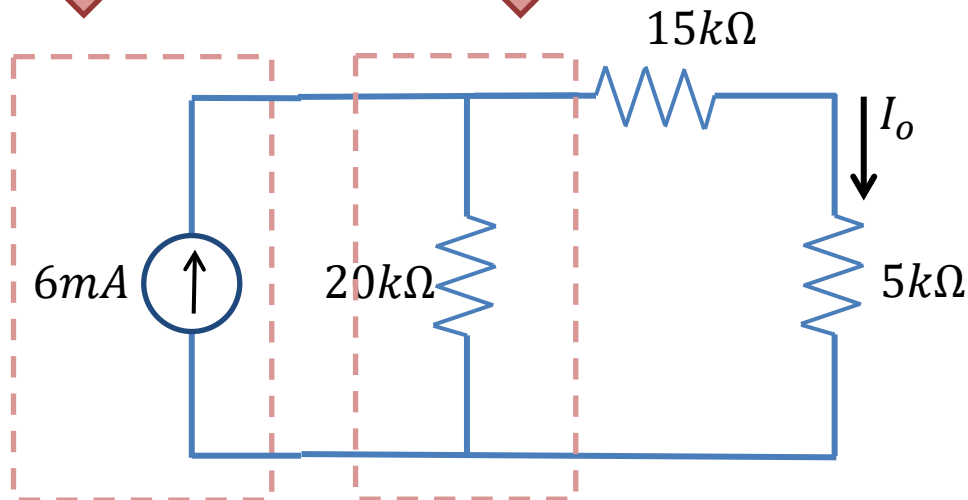

# Source Transformations

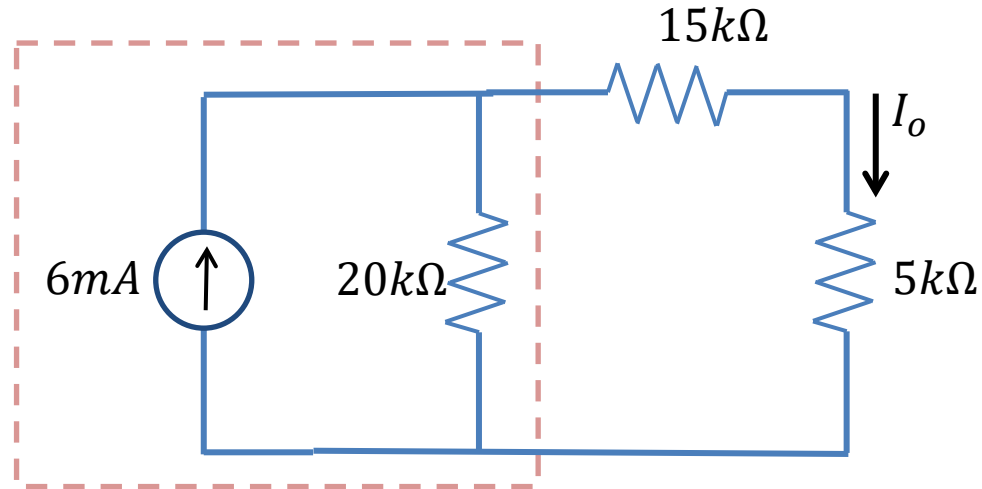



Transform current source

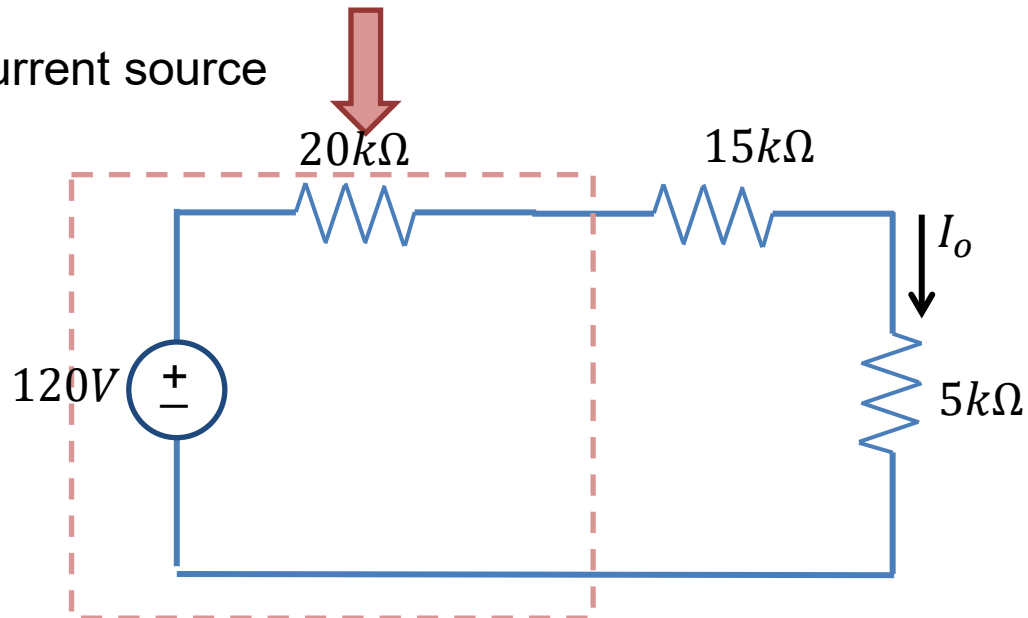

$$I_o = \frac{120\text{V}}{40\text{k}\Omega} = 3\text{mA}$$
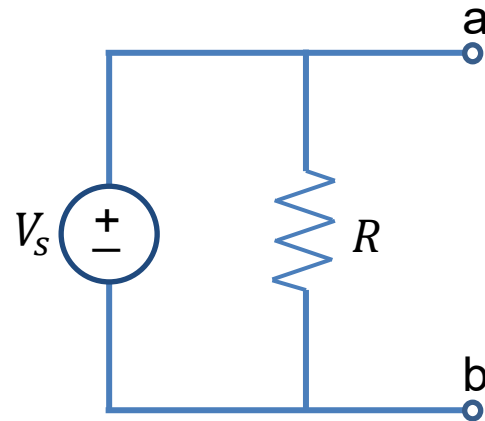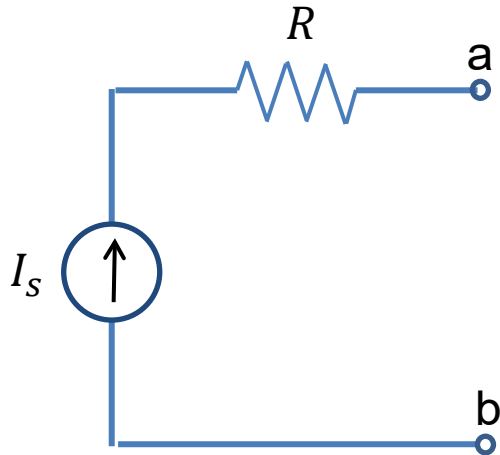
# Source Transformations


Before we present some examples, it is worth mentioning that we **DO NOT** use source transformations on the following circuits. **WHY NOT?**



**Q:** What can we do with the above circuits to simplify them? **Hint:** What role does the resistor  $R$  play in each circuit above?
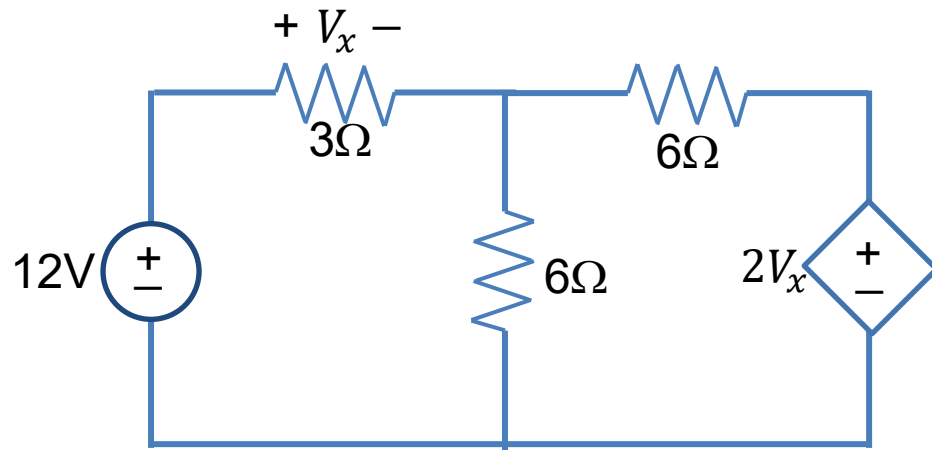
## Example

Find  $V_x$  by applying a sequence of source transformations.



**Note:** If the circuit has dependent sources, we need to make sure to preserve the element with the control voltage/current.