

First Order Circuits with AC Sources


In this set of notes, we examine the behavior of first order circuits with AC (sinusoidal) sources.

Suppose in the RC circuit shown, the input voltage is a sinusoid:

$$v_{in}(t) = A\cos(\omega t + \theta),$$

where

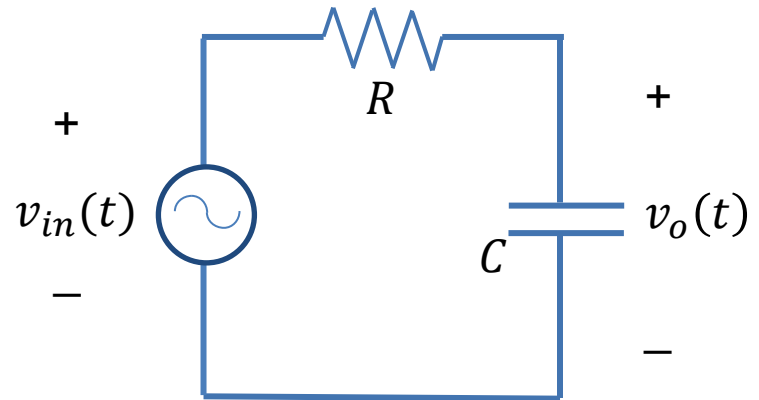A is the amplitude,
 ω is the frequency
(in radians per second) and
 θ is the phase of the sinusoid.



The differential equation that describes this circuit is:

$$RC \frac{dv_o}{dt} + v_o(t) = v_{in}(t)$$


First Order Circuits with AC Sources

$$RC \frac{dv_o}{dt} + v_o(t) = A \cos(\omega t + \theta),$$

The homogeneous solution to this equation is:

$$v_h(t) = B e^{-t/RC}.$$

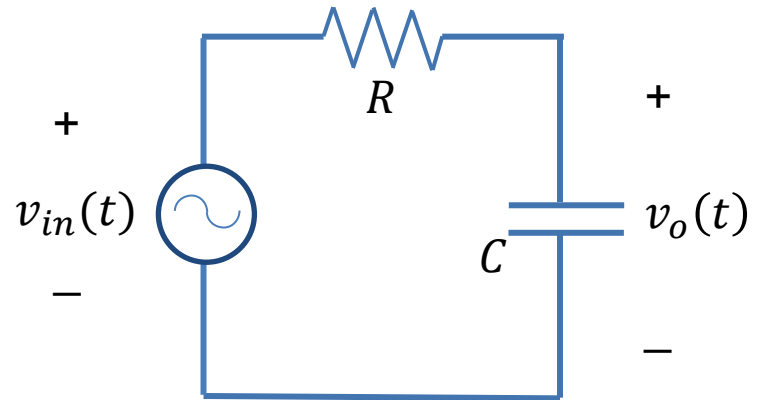To find the particular solution, use the method of undetermined coefficients.



Assume a particular solution of the form:

$$v_p(t) = D \cos(\omega t + \theta) + E \sin(\omega t + \theta).$$

Then

$$\frac{dv_p}{dt} = \omega E \cos(\omega t + \theta) - \omega D \sin(\omega t + \theta).$$


Plugging these into the differential equation produces:

$$\begin{aligned} &\omega R C E \cos(\omega t + \theta) - \omega R C D \sin(\omega t + \theta) \\ &+ D \cos(\omega t + \theta) + E \sin(\omega t + \theta) \\ &= A \cos(\omega t + \theta). \end{aligned}$$

First Order Circuits with AC Sources

$$RC \frac{dv_o}{dt} + v_o(t) = A \cos(\omega t + \theta),$$
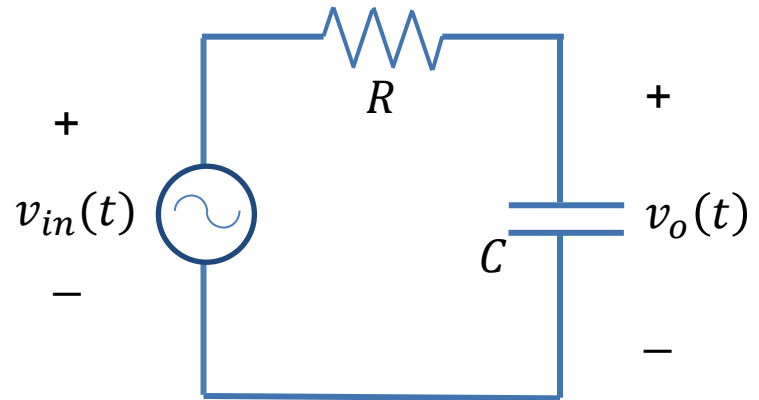
$$\begin{aligned} \omega RCE \cos(\omega t + \theta) - \omega RCD \sin(\omega t + \theta) \\ + D \cos(\omega t + \theta) + E \sin(\omega t + \theta) \\ = A \cos(\omega t + \theta). \end{aligned}$$



Equating coefficients of the $\cos()$ terms and coefficients of the $\sin()$ terms produces the following set of linear equations to solve for the constants D and E .

$$\begin{aligned} \omega RCE + D &= A \\ -\omega RCD + E &= 0 \end{aligned}$$

or in matrix form

$$\begin{bmatrix} 1 & \omega RC \\ -\omega RC & 1 \end{bmatrix} \begin{bmatrix} D \\ E \end{bmatrix} = \begin{bmatrix} A \\ 0 \end{bmatrix}$$

The solution to this set of equations is:


$$\begin{bmatrix} D \\ E \end{bmatrix} = \frac{A}{1 + (\omega RC)^2} \begin{bmatrix} 1 \\ \omega RC \end{bmatrix}$$

First Order Circuits with AC Sources

$$RC \frac{dv_o}{dt} + v_o(t) = v_{in}(t),$$

$$v_{in}(t) = A \cos(\omega t + \theta),$$

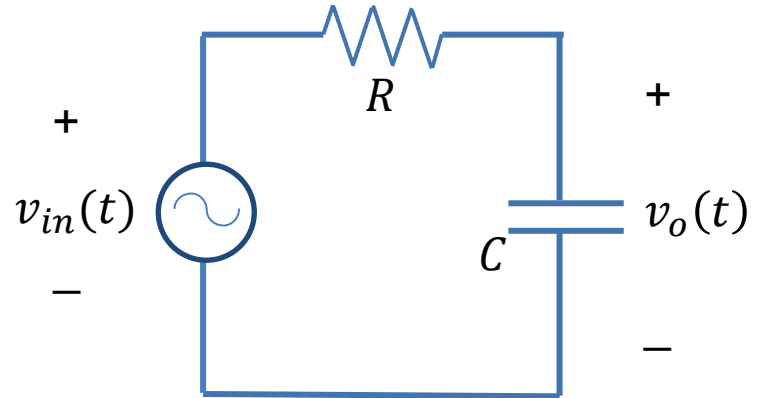Summarizing our results. The solution to this differential equation is



$$v_o(t) = B e^{-\frac{t}{RC}} + \frac{A \cos(\omega t + \theta)}{1 + (\omega RC)^2} + \frac{A \omega RC \sin(\omega t + \theta)}{1 + (\omega RC)^2}$$

Or by using a few trig identities, we can rewrite this in the following equivalent form:

$$v_o(t) = B e^{-\frac{t}{RC}} + \frac{A \cos(\omega t + \theta - \tan^{-1} \omega RC)}{\sqrt{1 + (\omega RC)^2}}$$

Quite often, we are not concerned with the transient part of the solution. In this case, the part of the output that remains is the sinusoidal part.


First Order Circuits with AC Sources

$$RC \frac{dv_o}{dt} + v_o(t) = v_{in}(t),$$

$$v_{in}(t) = A \cos(\omega t + \theta),$$

“Sinusoidal steady state” output:
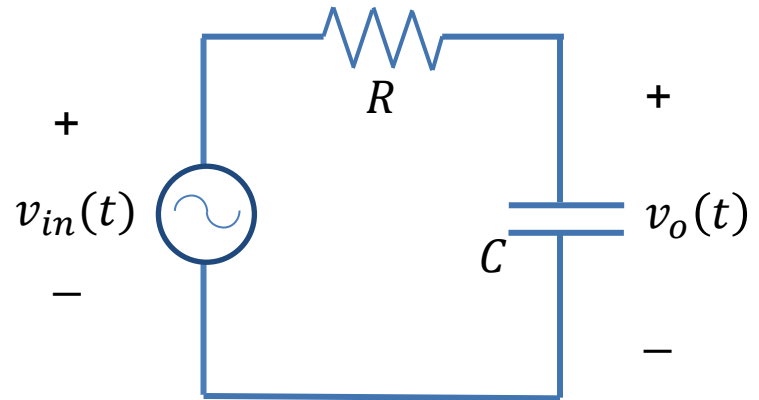
$$v_o(t) = \frac{A \cos(\omega t + \theta - \tan^{-1}(\omega RC))}{\sqrt{1 + (\omega RC)^2}}$$



Notice that the output voltage is a sinusoid of the same frequency as the input sinusoid. Furthermore:


- 1) The amplitude of the output has been scaled by a factor of $\frac{1}{\sqrt{1 + (\omega RC)^2}}$. This is known as the magnitude response of the circuit.
- 2) The phase of the output has been shifted by $-\tan^{-1}(\omega RC)$ radians. This is known as the phase response of the circuit.

First Order Circuits with AC Sources

Magnitude Response: $\frac{|v_o|}{|v_{in}|} = \frac{1}{\sqrt{1+(\omega RC)^2}}$

Phase Response:
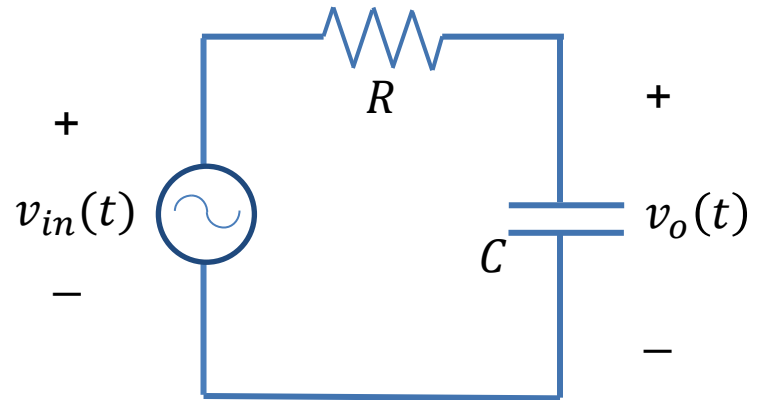
$$\angle v_o - \angle v_{in} = -\tan^{-1}(\omega RC)$$



For low frequency inputs, $\omega \ll 1/RC$, so that:

$$\frac{|v_o|}{|v_{in}|} \approx 1 \text{ and } \angle v_o - \angle v_{in} \approx 0.$$

For high frequency inputs, $\omega \gg 1/RC$, so that:

$$\frac{|v_o|}{|v_{in}|} \approx 0 \text{ and } \angle v_o - \angle v_{in} \approx -\frac{\pi}{2}.$$

This circuit is known as a *low-pass filter* since it allows low frequencies to pass but attenuates high frequencies.