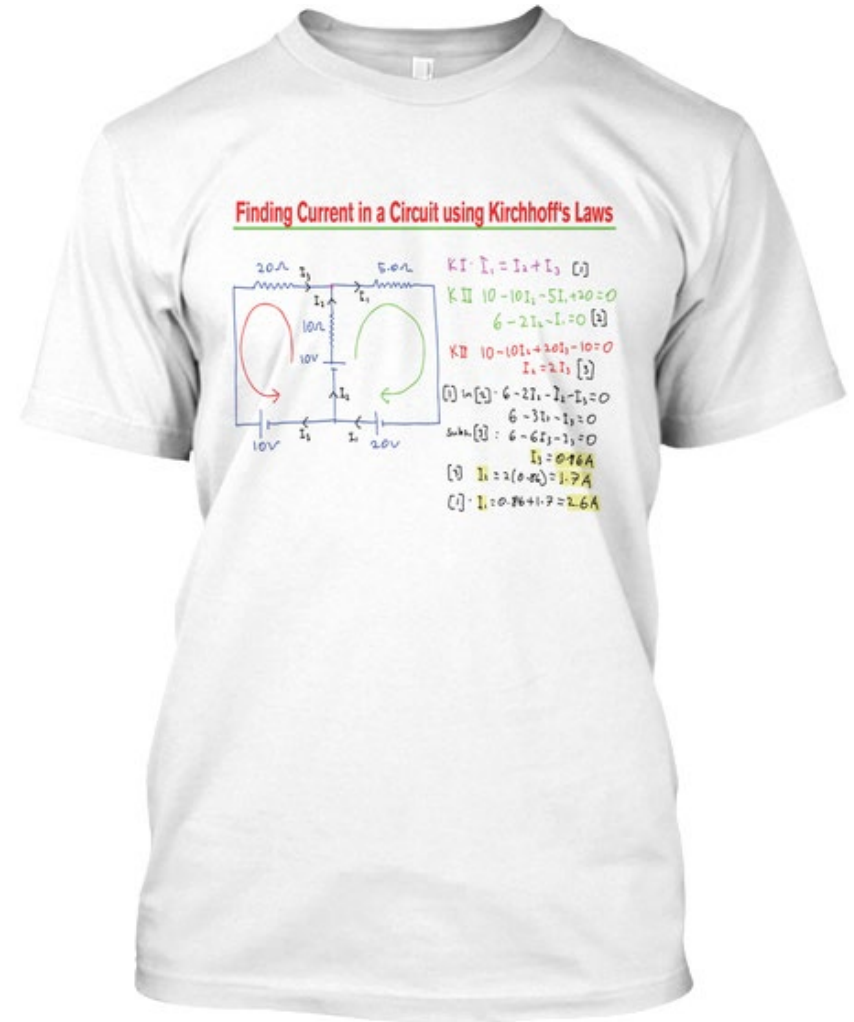


# Kirchoff's Laws


Kirchoff's Laws form the foundation of all circuit analysis tools and techniques.

- ✓ Kirchoff's Voltage Law (KVL) – The sum of all voltage drops around a closed loop in a circuit must be equal to zero.
- ✓ Kirchoff's Current Law (KCL) – The sum of all currents entering any node in a circuit must be equal to the sum of all currents leaving that same node.


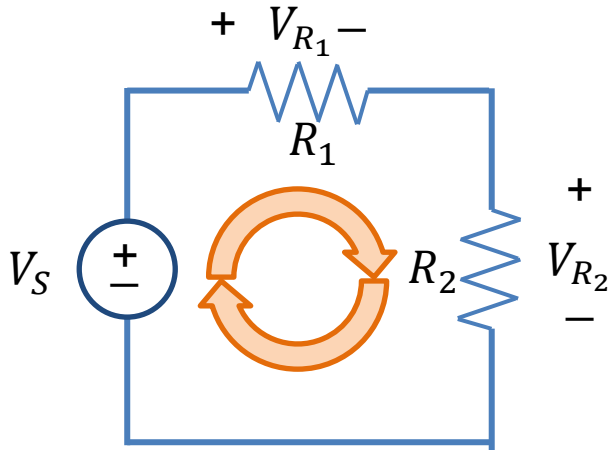
# Kirchoff's Laws

**Kirchoff's Voltage Law (KVL):** The sum of all voltage drops around any closed loop in a circuit must be zero.



$$-V_S + V_{R_1} + V_{R_2} = 0$$

or equivalently

$$V_S = V_{R_1} + V_{R_2}$$


**A Hiker's Analogy:** Suppose we were hiking over hilly terrain. As we move along the hiking trail, we keep track of the changes in elevation (analogous to voltage rises/drops in our circuit). If we hike along a trail that eventually loops back to the starting point, the sum of all the elevation changes we encounter along the way must be zero.

## Note:

- ✓ it doesn't matter where we start and end on the loop
- ✓ nor does it matter in which direction we traverse the loop.
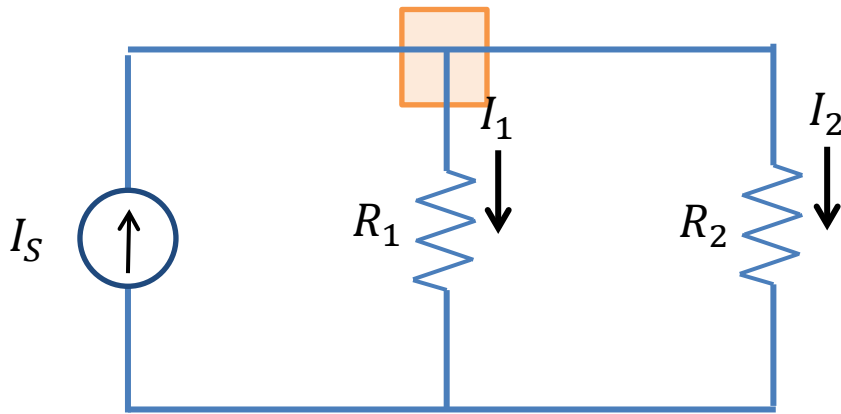
# Kirchoff's Laws

**Kirchoff's Current Law (KCL):** The sum of all currents entering (or leaving) any node of a circuit must be zero.



$$I_S - I_1 - I_2 = 0 \quad (\text{net flow in} = 0)$$


or equivalently

$$-I_S + I_1 + I_2 = 0 \quad (\text{net flow out} = 0)$$

or equivalently

$$I_S = I_1 + I_2 \quad (\text{flow in} = \text{flow out})$$

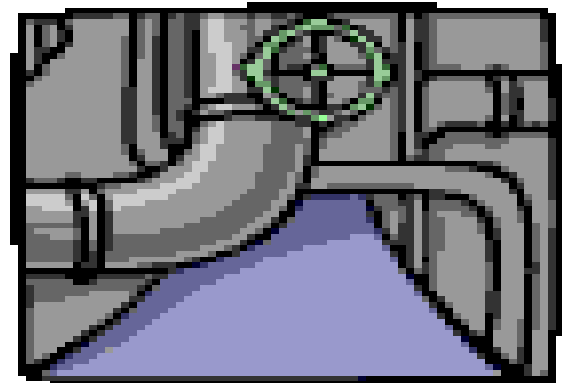**A Water Analogy:** Consider water flowing through a series of pipes. At any junction where multiple pipes intersect, the net flow into the junction must be zero.






# Example

For the circuit shown:

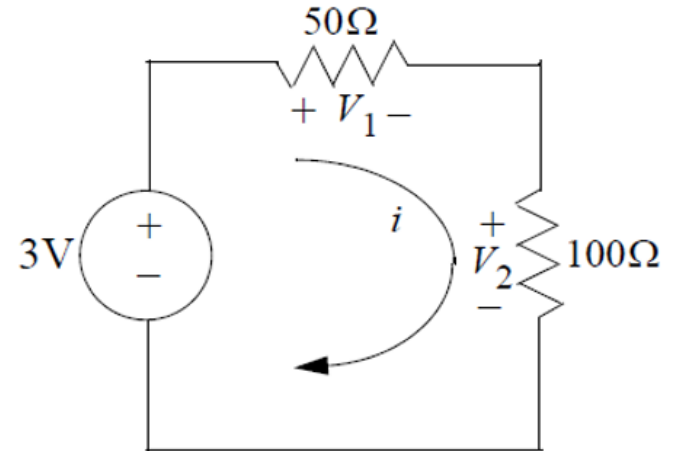- (a) Find the current flowing through the circuit.
- (b) Find the voltage across each resistor.






# Example

For the circuit shown:

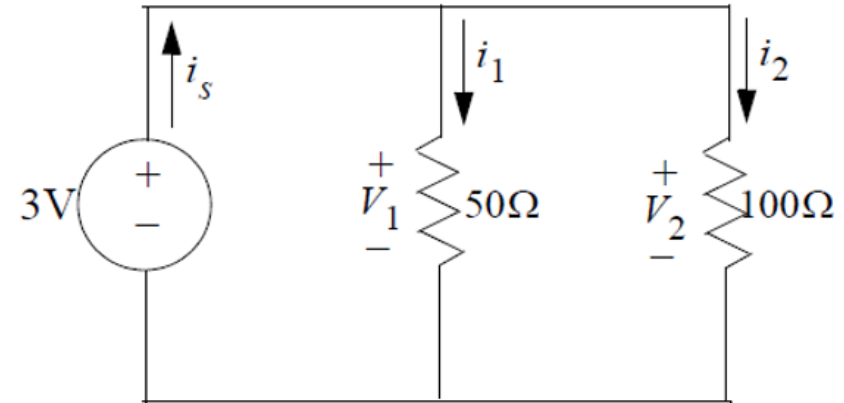- (a) Find the voltage drops across each resistor.
- (b) Find the currents flowing through each resistor.
- (c) Find the current flowing through the voltage source.





# Example

For the circuit shown, find all voltages and currents for the three resistors.

