

AC Circuit Analysis Using Phasors

If we were to analyze a circuit that is being driven by an AC source, we would expect to see a differential equation something like:

$$a \frac{d^2 y}{dt^2} + b \frac{dy}{dt} + cy(t) = d \cos(\omega t + \theta)$$

where $y(t)$ might be a voltage or a current.


The solution will consist of:

□ Homogeneous part

- Either underdamped, overdamped or critically damped.
- Transient → Will decay to 0 over time.

□ Particular part

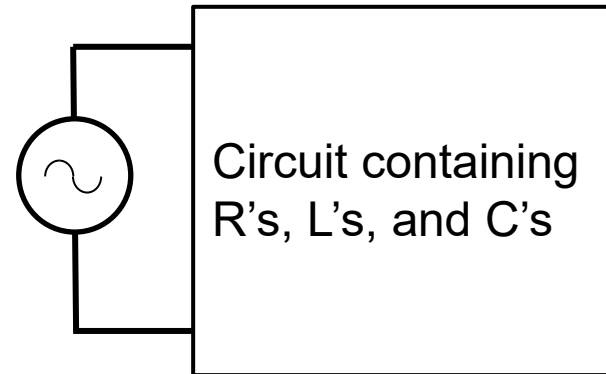- Something like
 $A \cos(\omega t + \theta) + B \sin(\omega t + \theta)$
- Persistent → does not decay over time.
- Sinusoidal (with same frequency as source)



With typical component values we use, the transient part will become insignificant after only small fractions of a second.

As a result, we are often interested in only the “steady state” part of the solution which is sinusoidal in nature.

We will use phasors/impedances to help us find the *sinusoidal steady state* solution to AC circuits.

AC Circuit Analysis Using Phasors

All of the techniques we use for the analysis of resistive circuits apply to circuits with Rs and Ls and Cs when we use phasors and complex impedances.

$$\text{KVL: } v_1(t) + v_2(t) + \cdots + v_n(t) = 0 \iff V_1 + V_2 + \cdots + V_n = 0$$

$$\text{KCL: } i_1(t) + i_2(t) + \cdots + i_n(t) = 0 \iff I_1 + I_2 + \cdots + I_n = 0$$

Series combinations of impedances: $Z_{eq} = Z_1 + Z_2 + \cdots + Z_n$.

Parallel combinations of impedances: $\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_n}$.


Voltage/current dividers, Δ -Y transformations, source transformations, Thevenin/Norton equivalents, node-voltage, mesh-current, etc.

AC Circuit Analysis Using Phasors

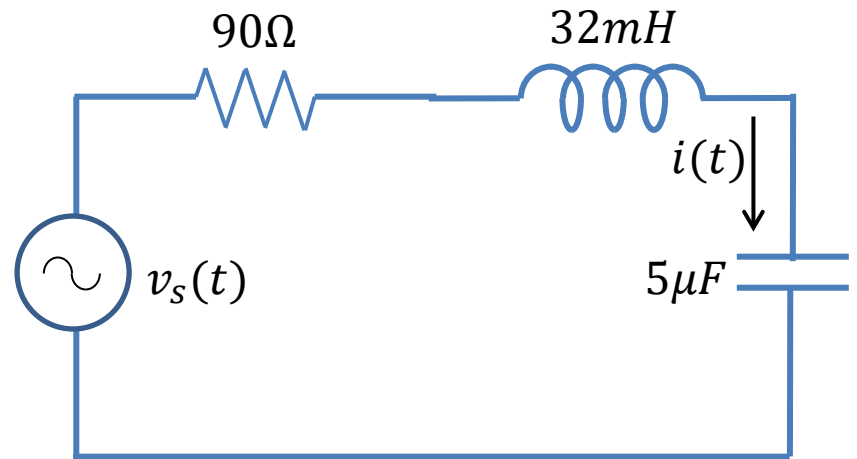Example:

Assuming

$v_s(t) = 750\cos(5000t + 30^\circ)$ volts,
find $i(t)$ in the circuit shown using
phasors.



AC Circuit Analysis Using Phasors

Example

Assuming $i_g(t) = 500\cos(2000t)$ mA, find $v_L(t)$ in the circuit shown using phasors.

